Verilog testbenches Proposed problems

Oprițoiu Flavius flavius.opritoiu@cs.upt.ro

October 15, 2023

Problem 1

Construct a Verilog module for a Full Adder Cell (FAC), and name it *fac*. The module has 3 1-bit inputs x, y and ci, and 2 1-bit outputs z and co. Write your code in a file called *fac.v*.

Construct a testbench that exhaustively verify the *fac* module implemented previously, and call it *fac_tb*. The content of the *fac_tb* module can be included in the same *fac.v* file, alongside the *fac* unit.

Build a script file, called *run_fac.txt*, for compiling, launching the simulation and running the simulation of the *fac_tb* module.

Using 2 *fac* instances, construct a 2-bit adder called *add2b*, having 2, 2-bit inputs x and y and the 1-bit input *ci*, together with the 2-bit output *o* and the 1-bit output *co*. Write your code in file *add2b*.*v*.

Construct a testbench module for verifying your implementation, called *add2b_tb* and the associated script file *run_add2b_txt*

Design a module cmp2b for comparison of 2-bit unsigned numbers, having 2, 2-bit inputs, x and y, for the 2 numbers to compare and 3 1-bit outputs: eq(equal), lt(less than) and gt(greater than). Write your code in file cmp2b.v.

Problem 5

Using module cmp2b, build a 4-bit comparator, called cmp4b, having 2, 4-bit unsigned inputs x and y, for the 2 operands and 3 1-bit outputs: eq, lt and gt. Write your code in file cmp4b.v.

Construct a testbench module for exhaustive verification of your implementation, called *cmp4b_tb* and the associated script file *run_cmp4b_txt*.

Problem 6

Build a module for addition of two integers represented in C1, called $c1_add4b$ which has 2, 4-bit inputs x, y and a 1-bit input ci generating at its output signals z on 4 bits (no carry out because of the end around carry).

Construct a testbench module for exhaustive verification of your implementation, called *c1add4b*_*tb* and the associated script file *run_c1add4b*.*txt*.