

# Iterated addition

Proposed problems

Oprîtoiu Flavius  
flavius.opritoiu@cs.upt.ro

September 18, 2023

## Problem 1

Starting from the architecture of a sequential multi-operand adder, build a structure for calculating the following sum:

$$\sum_{i=1}^{199} (3 * i - 2)$$


The module should be called, *mlopadd*, having inputs *clk*(1 bit), *rst\_b*(1 bit), *x*(on the required number of bits that allows connecting to it all values  $3 * i - 2, \forall 0 \leq i \leq 199$ ) and output *a*(on the required number of bits allowing for representing the above sum).

Your solution should include:

1. the script file, "run\_mlopadd.txt"
2. a testbench generating the input signals in such a manner to facilitates computation of the above sum.
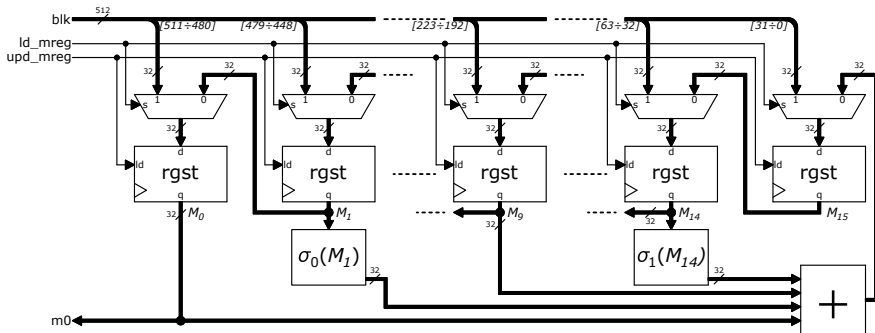
## Problem 2

Build the datapath component responsible for the message schedule of a SHA-256 architecture, depicted below:



The unit, called,  $mschdpath$  has inputs  $clk$  (1 bit),  $rst\_b$  (1 bit),  $ld\_mreg$  (1 bit),  $upd\_mreg$  (1 bit),  $blk$  (512 bits) and output  $m0$  (32 bits).

## Problem 2 (contd.)

The multiplexors on registers' input should be implemented as Verilog functions, as well as the  $\sigma_0$  and  $\sigma_1$  operators used by the message scheduler's data path.

Your solution should include:

1. the Verilog code
2. the script file, "run\_mschdpath.txt"
3. a testbench generating inputs as in the timing diagram bellow

