

# Writing parameterized modules

Opritoiu Flavius  
flavius.opritoiu@cs.upt.ro

September 18, 2023

# Introduction

Objectives:

- ▶ Datapath and control path separation
- ▶ Understand how to write parameterized modules

## *Datapath*

- Consists of elements processing the data: no decisions are taken
- Typical components: multiplexers, registers, Arithmetic and Logic Units (ALUs), counters
- Construct shared buses using three-state drivers

## *Control path*

- Concerned with decision making
- Described in terms of state machines

**Note:** State-enabled components (such as registers, counters) can be part of the datapath, as well.

## Reusable modules

Reusable modules are defined in terms of *parameters*, which can be redefined. In Verilog 2001 the module's parameters are specified in a dedicated section, marked by #( and ) symbols.

The code bellow describes a parallel load register with parameterized width (no. of bits) and initialization value (register content after reset or clear).

```
1  module rgst #(
2      parameter w = 8,           //register's width parameter; default of 8
3      parameter iv = {w{1'b0}} //initialization value parameter
4  )(
5      input  clk ,
6      input  rst_b ,             //asynchronous reset; active low
7      input  [w-1:0] d,         //input data, on w bits
8      input  ld ,               //synchronous load; active high
9      input  clr ,             //synchronous clear; active high
10     output reg [w-1:0] q      //register's content, on w bits
11 );
12
13     always @ (posedge clk , negedge rst_b)
14         if (!rst_b)
15             q <= iv; //set content to initialization value
16         else if (clr)
17             q <= iv; //set content to initialization value
18         else if (ld)
19             q <= d;
20 endmodule
```

## Reusable modules (contd.)

In-line, explicit redefinition of module's parameters, in Verilog 2001, uses the following format:

```
module-name #(parameter-name(value), ...)  
    instance_name (port-name(signal), ...)
```

Code bellow instantiate a 16-bit register, with an initialization value of 0

```
1 rgst #(  
2     .w(16)  
3 ) registru1 (  
4     .clk(clk), ...  
5 );
```

Code bellow instantiate a 4-bit register, initialized 15

```
1 rgst #(  
2     .w(4),  
3     .iv(4'd15)  
4 ) registru2 (  
5     .clk(clk), ...  
6 );
```

# Solved problem

## Constructing a register file using discrete registers

*Exercise:* Construct a 4x8 register file.

*Solution:* An  $M \times N$  *register file* is a storage element organized as an array of  $M$  registers, each register having  $N$  bits. It permits simultaneous reading one internal register and writing one internal register (possibly the same).

A register file's interface includes the following connections:


- an  $N$ -bit data input, for writing internal registers ( $wr\_data$ )
- an  $N$ -bit data output, for reading internal registers ( $rd\_data$ )
- an input address, selecting the register to be written ( $wr\_addr$ )
- an output address, selecting the register to be read ( $rd\_addr$ )
- data write enable signal ( $wr\_e$ )
- data read enable signal ( $rd\_e$ )

The enable lines of the writing/reading port are optional.  $M$  is, typically, of form  $2^k$ : the input/output addresses use  $k$  bits.

## Solved problem (contd.)
 
### Constructing a register file using discrete registers

The interface of a  $4 \times n$  register file is depicted bellow




For this case, the interface is made up of:

- the writing port ( $wr\_data$ ,  $wr\_addr$ ,  $wr\_e$ )
- the reading port ( $rd\_data$ ,  $rd\_addr$ ,  $rd\_e$ )
- clock signal ( $clk$ )
- reset signal ( $rst\_b$ )

# Solved problem (contd.)
 
## Constructing a register file using discrete registers


An 4x8 register file with no output enable line:



**Note:** The clock and reset lines were omitted for brevity.
 
## Three-state driver

Used for connecting several components on a shared line or bus.



Output  $o$  is set to  $i$  when enable line,  $e$ , is active, and to *high impedance* otherwise. An output set to high impedance (symbolized by  $z$ , in Verilog) allows other component to drive the logic level of the shared line or bus it connects to.

The code fragment bellow demonstrates commanding a signal into high impedance by a control line,  $e$ :

```
1  wire [15:0] data , data_hiz ;  
2  assign data_hiz = (e) ? data : 16'bz ;
```


Because the high impedance symbol,  $z$ , is the most significant bit of the constant in line 2, it is extended to 16 high impedance bits.



# Solved problem
 
## Constructing a multiplexer using three-state drivers

An  $n$ -bit 4-to-1 multiplexer, implemented with three-state drivers:



Multiplexer's select input,  $s$ , drives a 1-out-of-4 decoder. The final stage connects all three-state drivers' outputs together.