- 1. Perform the following arithmetic operations in binary, considering integer, unsigned operands:
  - a. 975 + 795 b. 975 - 795 c. 338 + 211 d. 338 - 211
- 2. Implement the following functions as Sum of

Products using the minimum number of logic gates:

a.  $f_1 = \sum (0, 2, 5, 6, 8, 10, 13, 15)$ b.  $f_2 = \sum (0, 2, 4, 8, 10, 14) + \sum_d (5, 6, 7, 12)$ c.  $f_3 = \sum (0, 1, 2, 3, 4, 9) + \sum_d (10, 11, 12, 13, 14, 15)$ d.  $f_4 = \prod (0, 2, 3, 4, 8, 10, 11)$